

**1.5.5** Repeat Problem 1.5.4 with  $v(t) = 10 \cos(120\pi t + 45^\circ)$ .

From **1.5.4**, we know that

$$Z = 10 + j \left( 12\pi - \frac{1}{0.12\pi} \right)$$

Now we rewrite the input signal in phasor notation, compute the current phasor, and then convert that phasor back to a signal in the time domain.

$$\begin{aligned} V(\chi) &= 10e^{j\frac{\pi}{4}} \\ &= 10 \cos \frac{\pi}{4} + j10 \sin \pi/4 \\ &= 10 \frac{\sqrt{2}}{2} + j10 \frac{\sqrt{2}}{2} \\ &= 10 \frac{\sqrt{2}}{2} (1 + j) \end{aligned}$$

$$\begin{aligned} I(\chi) &= \frac{V(\chi)}{Z} \\ &= \frac{10 \frac{\sqrt{2}}{2} (1 + j)}{10 + j \left( 12\pi - \frac{1}{0.12\pi} \right)} \\ &\approx 0.240 - j0.133 \end{aligned}$$

$$\begin{aligned} i(t) &= \sqrt{(0.240)^2 + (-0.133)^2} \cos \left( 120\pi t + \tan^{-1} \left( \frac{-0.133}{0.240} \right) \right) \\ &= 0.274 \cos (120\pi t - 0.506) \\ &= 0.274 \cos (120\pi t - 29^\circ) \text{A} \end{aligned}$$

This is practically the same result as **1.5.4**, except that the signal is shifted forward by about  $45^\circ$ , as expected.